



Credit Hours System

ELCN321



Cairo University

Faculty of Engineering

VLSI

ANALOG PROJECT

Submitted to: Dr. Mohamed Refky

Student name: Hosam Moetaz Hosam

Student ID: 1180534

Submission Date: 25/12/2021

IMPLEMENTATION FOR P-MOS

Date / / Object

Hossam Moctar Hossam
1180534

VLSI
Analog project

□ For P-Mos transistors

↳ each transistor is of $\frac{40\mu m}{1\mu m}$ \rightarrow each is of width $40\mu m$


\therefore we have total width of $120\mu m$ (length $\rightarrow 1\mu m$)

↳ The stack consists of the 3 pmos

we will use $k=12 \rightarrow$ we will use 12 number of fingers

\therefore The width of the stack is $\frac{120\mu m}{12} = 10\mu m$

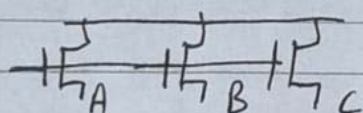\therefore Assume the name of the 3 transistors are A, B, C



\therefore gate size of $\frac{10\mu m}{1\mu m}$
(poly)


\therefore each transistor is of 4 fingers and the size of the finger is $\frac{10\mu m}{1\mu m}$

And we will use interdigitation technique for matching


A A B B C C C C B B A A
S D S D S D S D S D S D

- * All of them have similar source
- * All of them have similar gate

We will use first method shown below

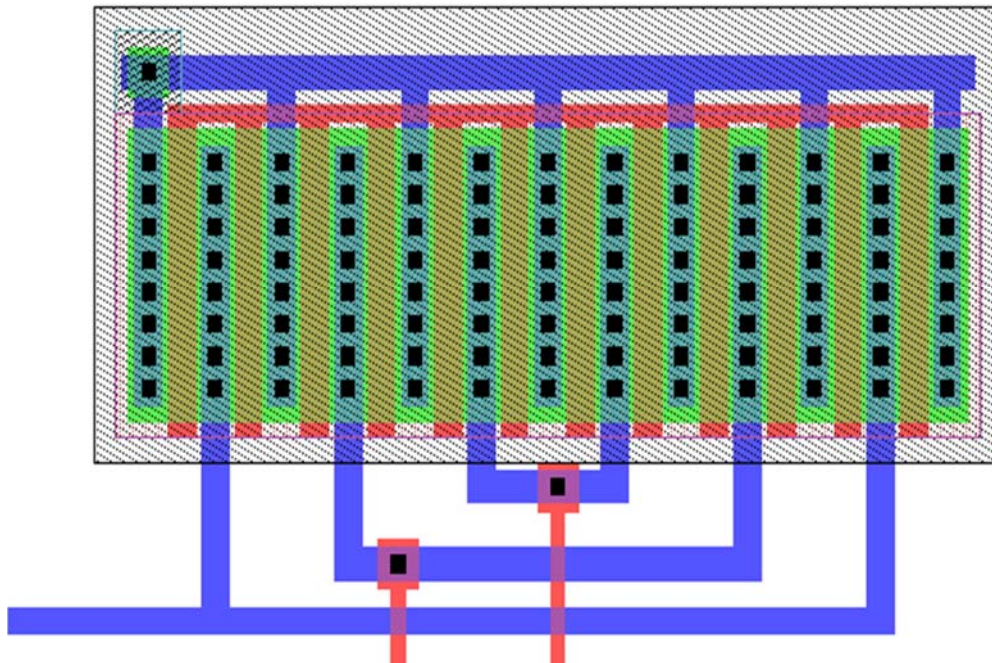

Can also be implemented by using metal 2

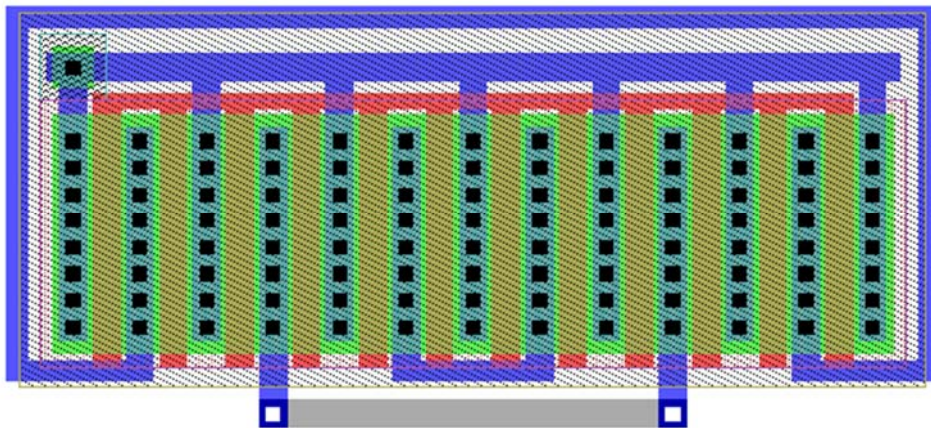

IMPLEMENTATION FOR RESISTOR

12] For resistors

Date	/	/	Object
------	---	---	--------

→ we implemented a unit resistor of $2k\Omega$ and it's of a linear type

∴ we used an N-well resistor with a sheet resistance of $2k\Omega/\square$

↳ instead of using poly type resistor with a sheet resistance of $25 \Omega/\square$
↳ it will require very large area in our case

∴ we implement an N-well resistor
 ↳ $2K\Omega$ (with w and $L = 12.5 \times 12.5$)
 ↳ N-well in our case is used to minimize area

→ we will use inter digitation technique for matching

$$R_D = 10 \times 2k$$
$$R_1 = 50 \times 2k, R_1 = 50 \times 2k$$
$$R_L = 100 \times 2k$$

} stack
→ containing
these resistance

\therefore we have a total $210 \times 2\pi$

\therefore we will use 42 pins in our case

$$\therefore R_b = \frac{10}{210} \times 42 = \underline{2 \text{ finger}}$$
$$R_1 = \frac{50}{210} \times 42 = 10 \text{ Pinger}$$
$$R_L = \frac{100}{210} \times 42 = 20 \text{ finger}$$

where each finger
is made of
 $5 \times 2k$ Ω //

$$\Rightarrow R_D R_1 R_L R_1 R_L R_1 R_L R_1 R_L R_1 R_L R_1 R_L R_1 R_L R_1 R_L \rightarrow$$

Complementation of N-well resistance is shown in the following figure.

K.M.S.



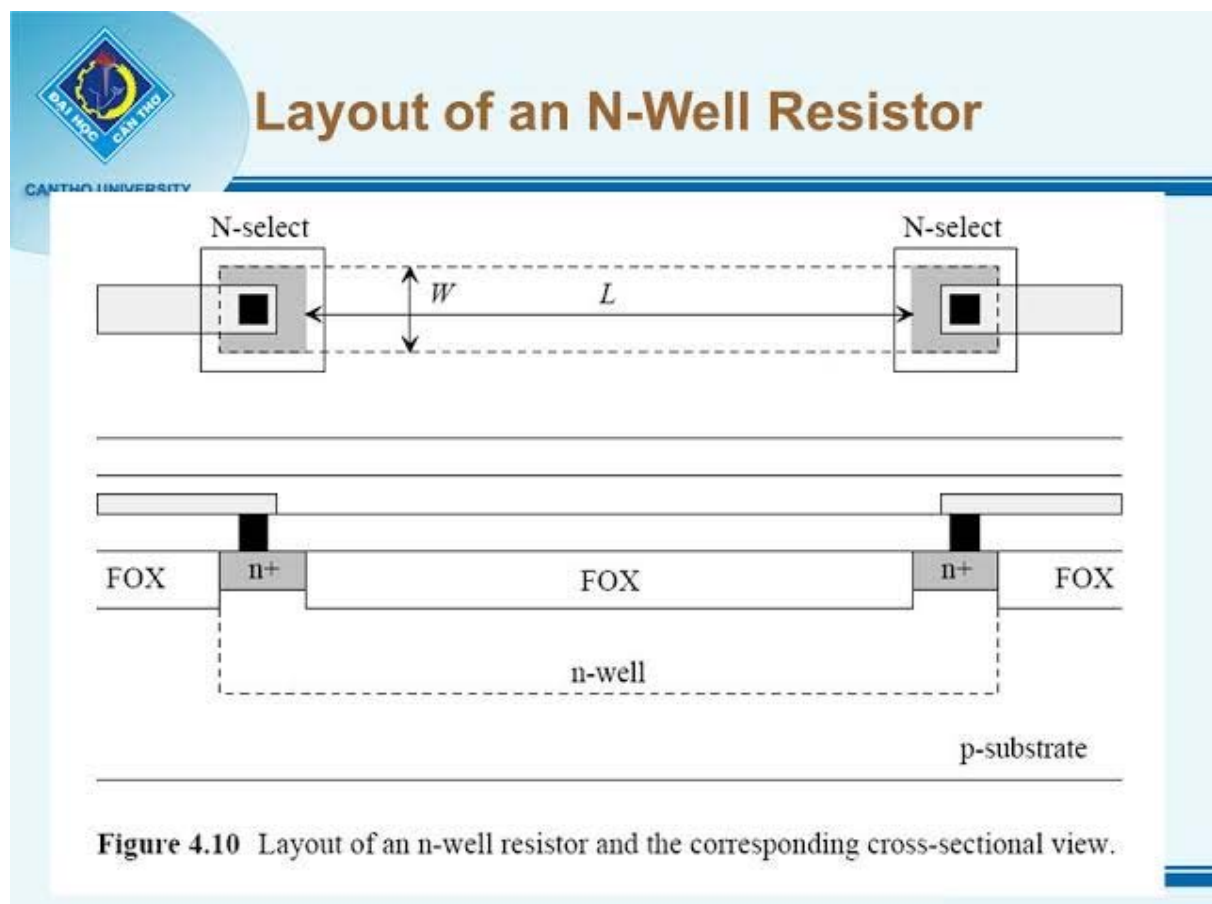
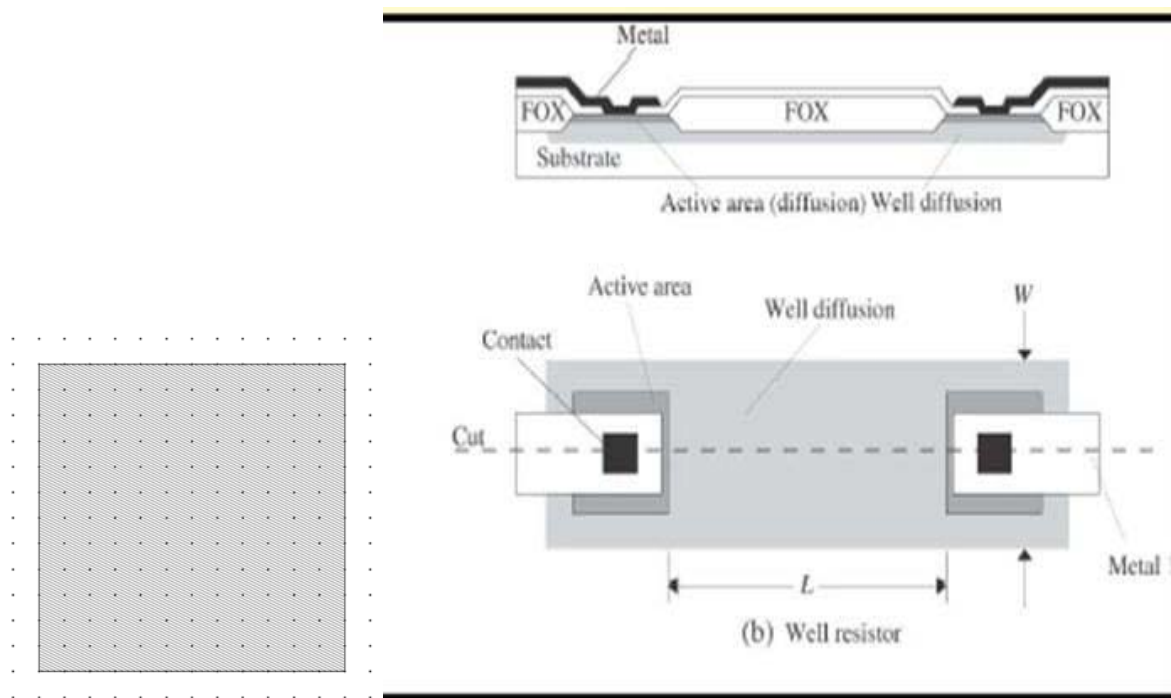


Figure 4.10 Layout of an n-well resistor and the corresponding cross-sectional view.

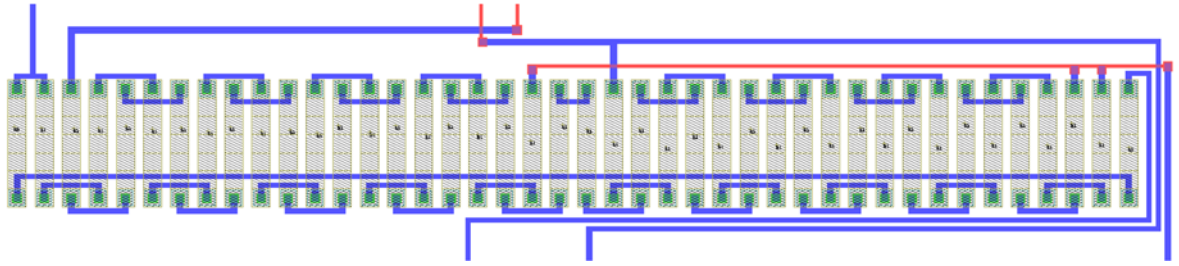


IMPLEMENTATION FOR N-MOS

[3] For N-MOS we can use fingers to minimize C_{DB} and C_{SB} (parasitic capacitance)
 we will assume x is of $10\mu\text{m}/1\mu\text{m}$ similar ratio as for P-MOS
 \therefore we have a total width of $90\mu\text{m}$
 \therefore we will use 9 fingers
 so gate size similar to P-MOS = $\frac{10\mu\text{m}}{1\mu\text{m}}$ (poly)
 \therefore transistor of $8x \rightarrow$ we will use 8 fingers
 transistor of $1x \rightarrow$ we will use 1 finger
 * both have similar source so matching is required
 \therefore we only used fingers to reduce capacitance

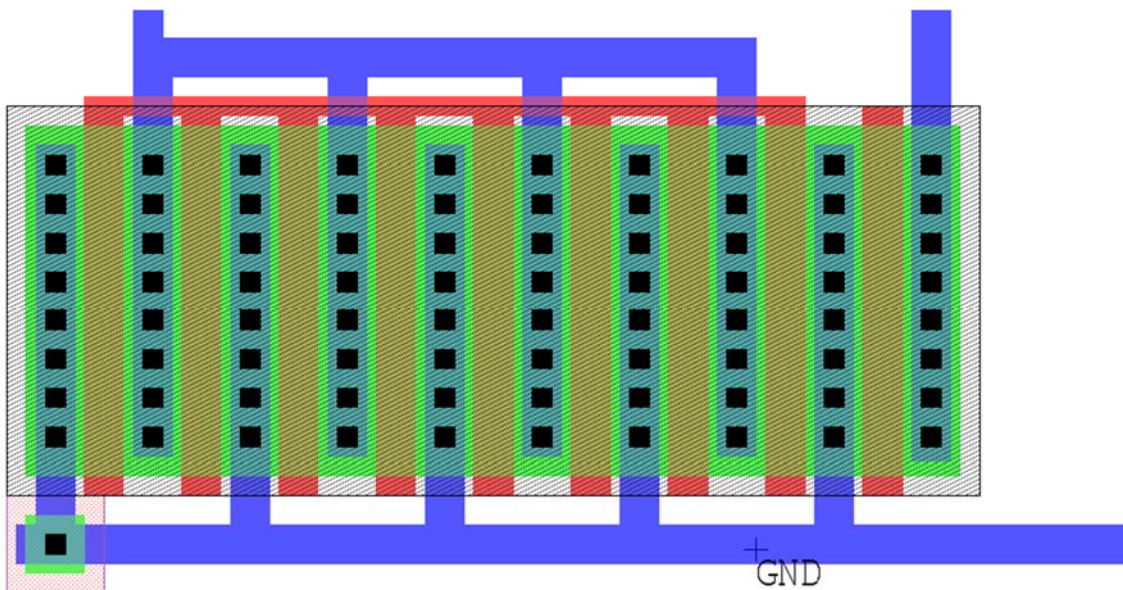


COMPLETE DESIGN:

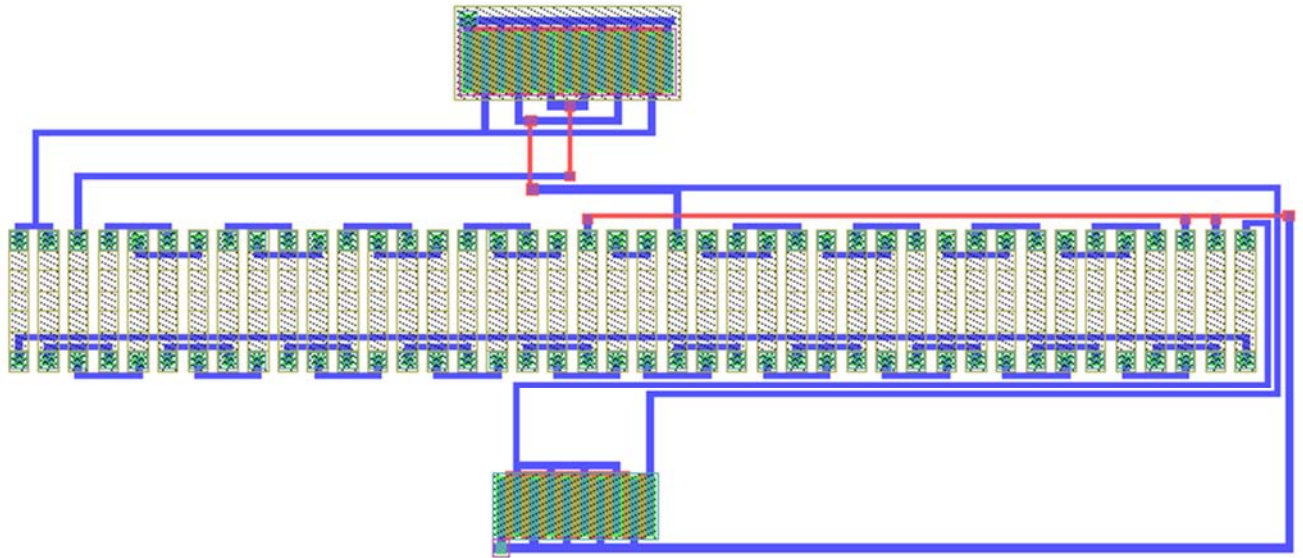

ANOTHER WAY TO IMPLEMENT A RESISTOR

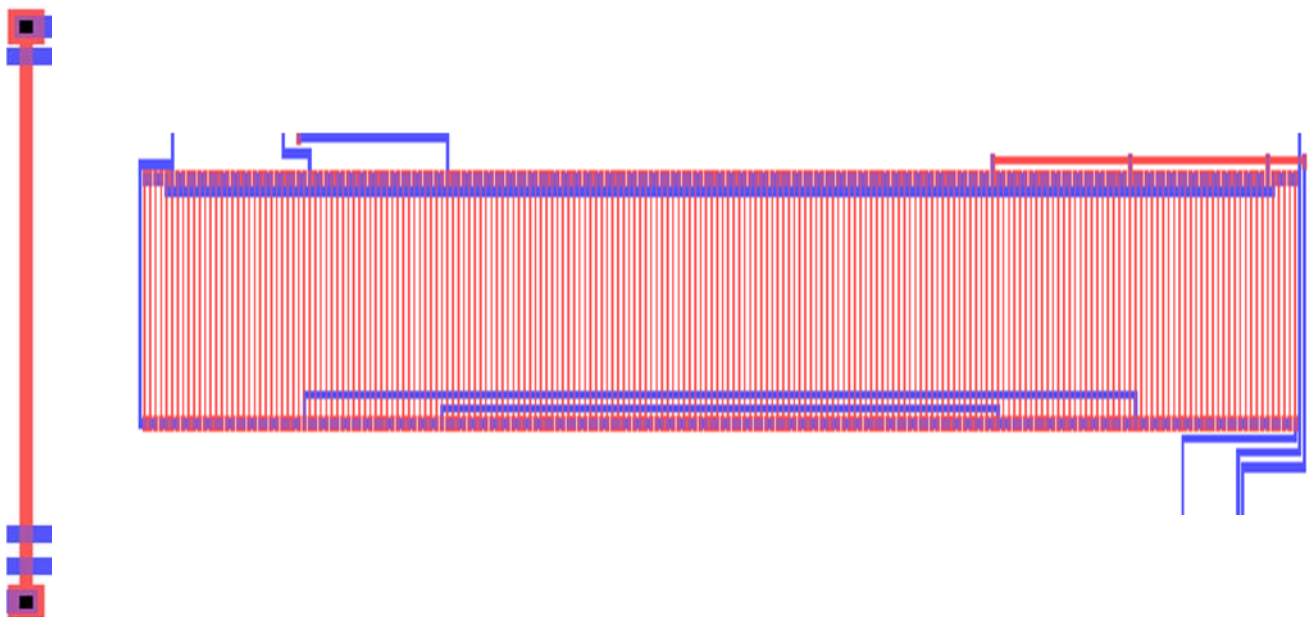This is the size of single unit resistor of 2k ohm



Date / / Object _____

→ we can also implement resistor using poly
 but it will result in large area as shown
 ↳ sheet resistance for poly is $40\text{-}\Omega/\square$
 ∴ in order to implement $2\text{K-}\Omega$ resistance
 we would require 50 mils

∴ we will use interdigitated technique for matching
 ∴ we have a total of $210 \times 2\text{K-}\Omega$
 ↳ we will use 210 fingers
 ↳ where each finger is of $2\text{K-}\Omega$

∴ $R_D = 10\text{ finger}$, $R_1 = 50\text{ finger}$
 and $R_L = 100\text{ finger}$

will be implemented as follow:

$R_D(5)$ $R_1(25)$ $R_1(25)$ $R_L(100)$ $R_1(25)$ $R_1(25)$ $R_D(5)$

Complete design for this method

